PROJECT

Name: Farabi Gulandaz


ID: 021 182 026

Course Title: Electrical Wiring and Drafting


Course Code: EEE 220


Section : A


Date: 13. 01. 21

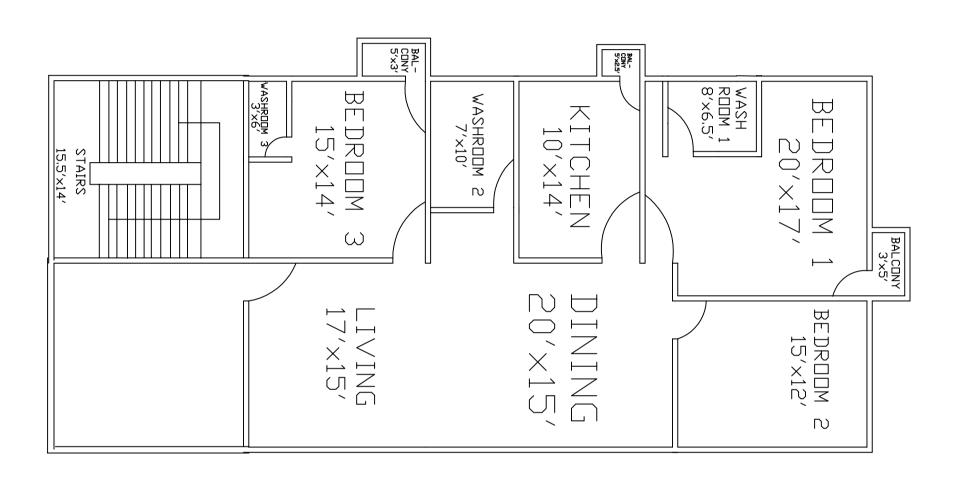

TotalSpace= 55' x 32' = 1760 sq feet

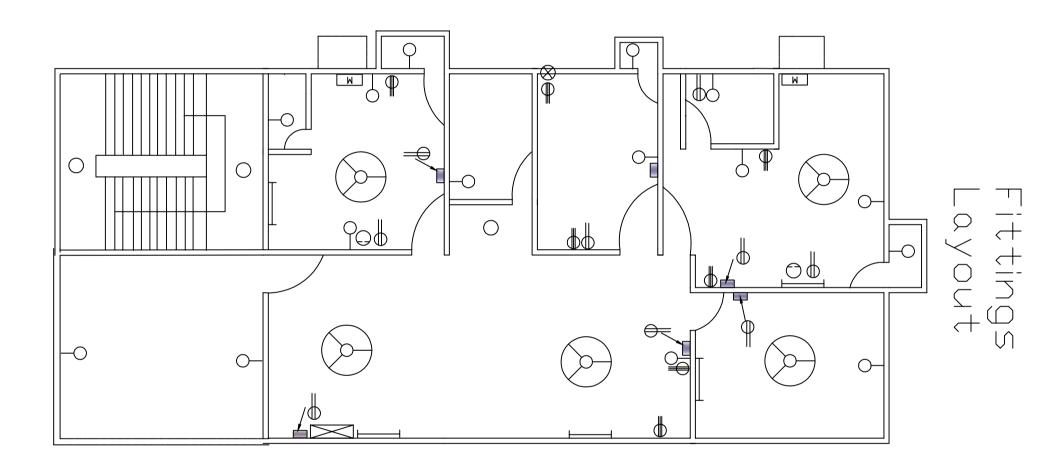

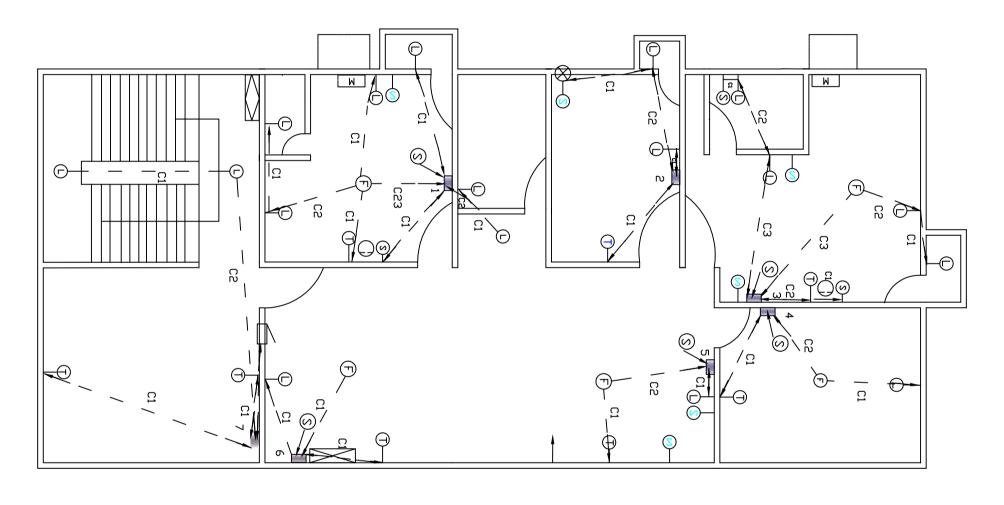

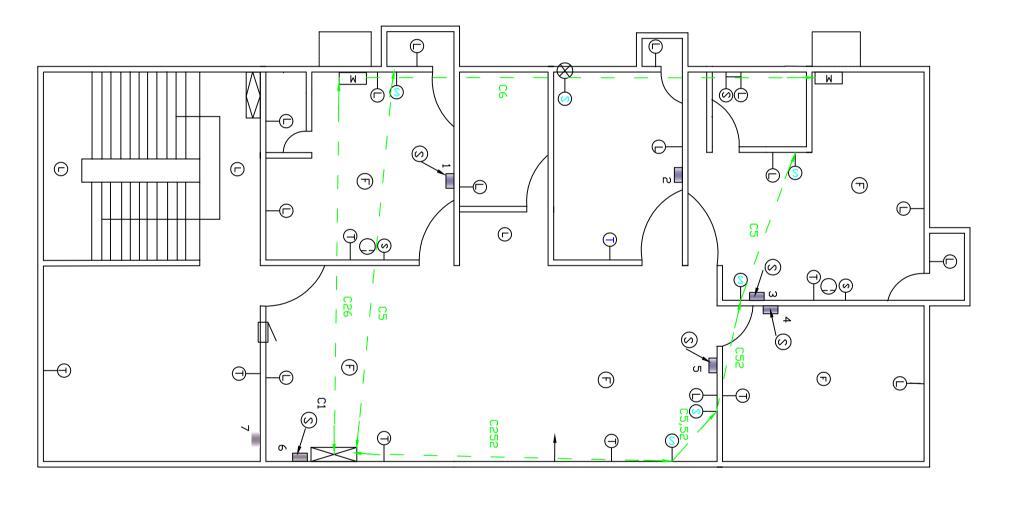

Calculation for Switch Board

SB 01	<u>SB 02</u>	<u>SB 03</u>	
5L= 5* 26 = 130 W 1T= 1*40 = 40 W 1F= 1*80 = 80 W 1TS= 1*500= 500 W 1SS= 1*500= 500 W 1K = 1*60 = 60 W	2L= 2* 26 = 52 W 1SL= 1*500= 500 W 1ST= 1*500= 500 W	4L= 5* 26 = 104 W 1T= 1*40 = 40 W 1F= 1*80 = 80 W 1TS= 1*500= 500 W 1SS= 1*500= 500 W 1ST= 1*500= 500 W	
1310 W	1052 W	1310 W	
$P=VI\cos\theta$ $Cos\theta=1$ $I=P/V\cos\theta$ $=1310/240$ $=5.46 A$	$P=VI\cos\theta$ $Cos\theta=1$ $I=P/V\cos\theta$ $=1052/240$ $=4.38 A$	$P=VI\cos\theta$ $Cos\theta=1$ $I=P/V\cos\theta$ $=1724/240$ $=7.18 A$	
<u>SB 04</u>	<u>SB 05</u>	<u>SB 06</u>	
1L= 1* 26 = 26 W 1T= 1*40 = 40 W 1F= 1*80 = 80 W 1SS= 1*500= 500 W	1L= 1* 26 = 26 W 1T= 1*40 = 40 W 1F= 1*80 = 80 W 1SS= 1*500= 500 W	1L= 1* 26 = 26 W 1T= 1*40 = 40 W 1F= 1*80 = 80 W 1SS= 1*500= 500 W	
646 W	646 W	646 W	
P= VIcosθ Cosθ= 1	P= VIcosθ Cosθ= 1	$P=VI\cos\theta$ $Cos\theta=1$	
I= P/Vcosθ = 646/240 =2.69 A	I= P/Vcosθ = 646/240 =2.69 A	I= P/Vcosθ = 646/240 =2.69 A	

Calculation for Switch Board

SB 07

$$2K = 2*60 = 120 W$$

 $2T = 2*40 = 80 W$


200 W

$$P = VI\cos\theta$$

 $\cos\theta = 1$

$$I = P/V\cos\theta$$
$$= 200/240$$

=0.83 A

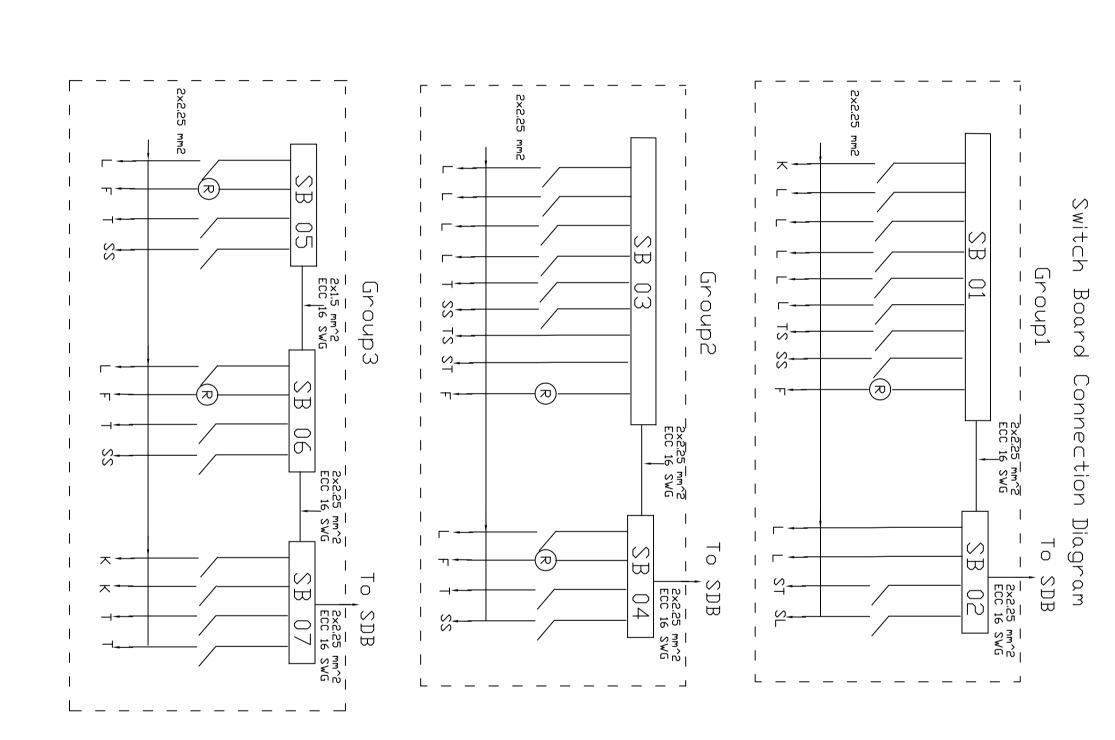

Calculation of Switch Board Grouping

Group 1	Group 2	Group 3	
SB= SB 01, SB 02	SB= SB 03, SB 04	SB= SB 05, SB 06, SB 07	
I= 5.46A + 4.38A = 9.84 A	I= 7.18 A + 2.69A = 9.87 A	I= 2.69A + 2.69A + 0.83A = 6.21 A	
MCB rating= 10 A	MCB rating= 10 A	MCB rating= 10 A	

Calculation of SDB

$$PLL = 1310 + 1052 + 1724 + 646 + 646 + 646 + 200 = 6224 \ W$$

$$P_{HL-15} = 5*1000 = 5000 W$$

$$P_{HL-20} = 2*2250 = 4500 W$$

$$P_{total} = (6224 * 0.6) + (5000*0.7) + (4500*1)$$
$$= 11734.4 \text{ W} = 11.7 \text{ kW} > 9 \text{ kW}$$

Therefore, 3-Ø and 415 V L-L is used.

$$I = (11.7*1000) / (1.73*415*0.9) = 18.09 A$$

With spare and safety factor,


$$I = (18.09+10) * 1.25 = 35.11 A$$
$$= 40A MCB$$

Calculation of MDB


- 10 stored building each floor has 1 unit.
- One 3hp pump and one 10 hp elevator

$$\begin{aligned} P_{\text{Biulding}} &= (11.7*1000*10) + (3*745.7) + (10*745.7) \\ &= 126.7 kW \end{aligned}$$


Distribution Connection

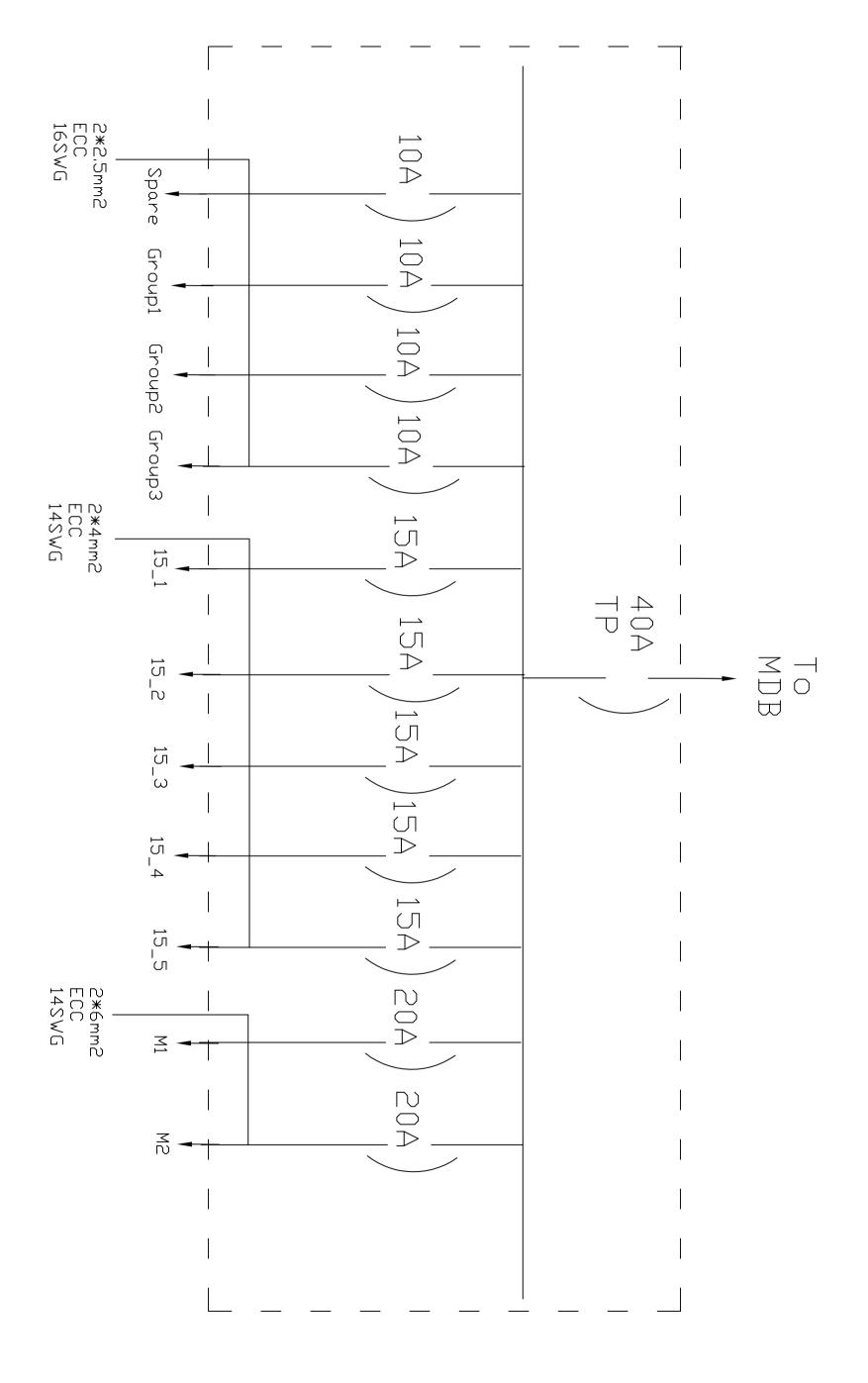

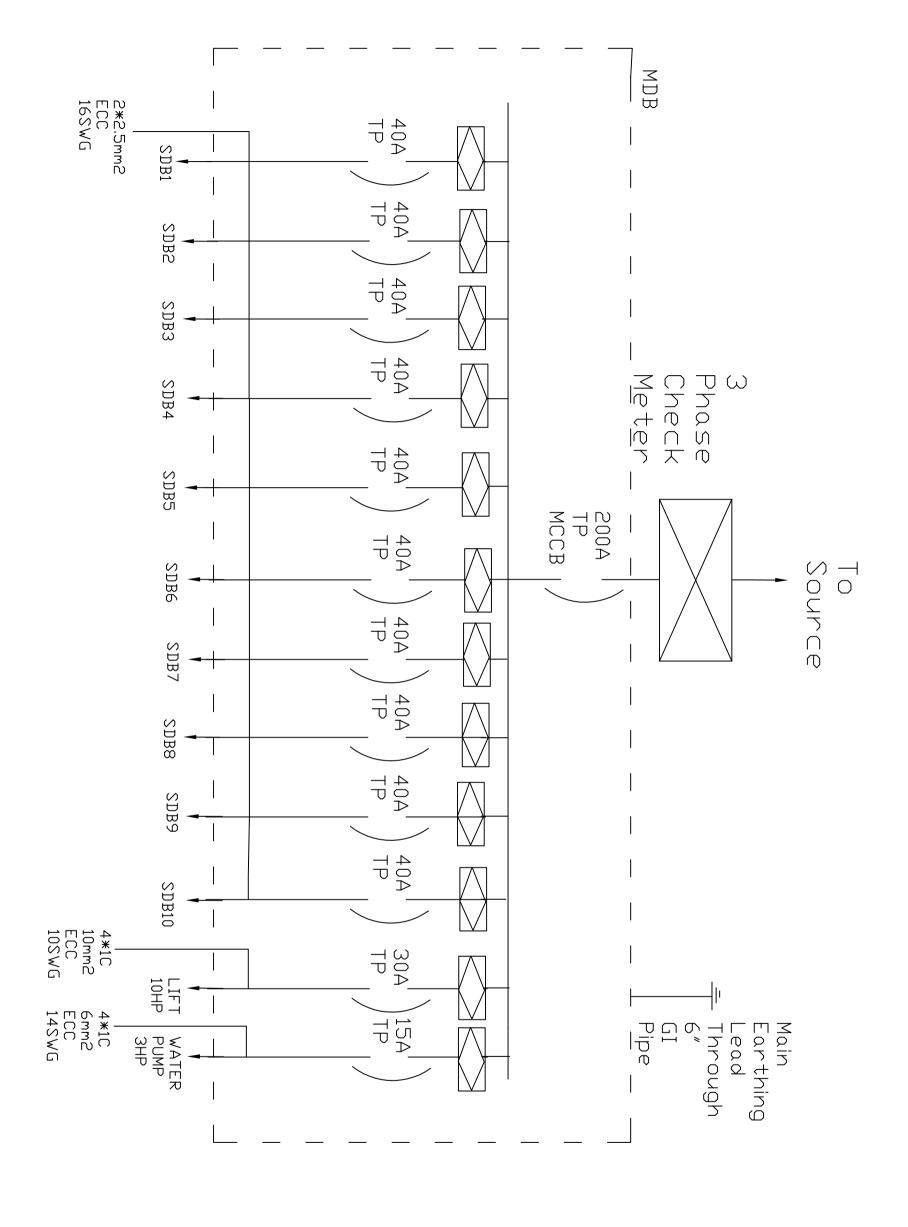Main Distribution Board Connection Diagram



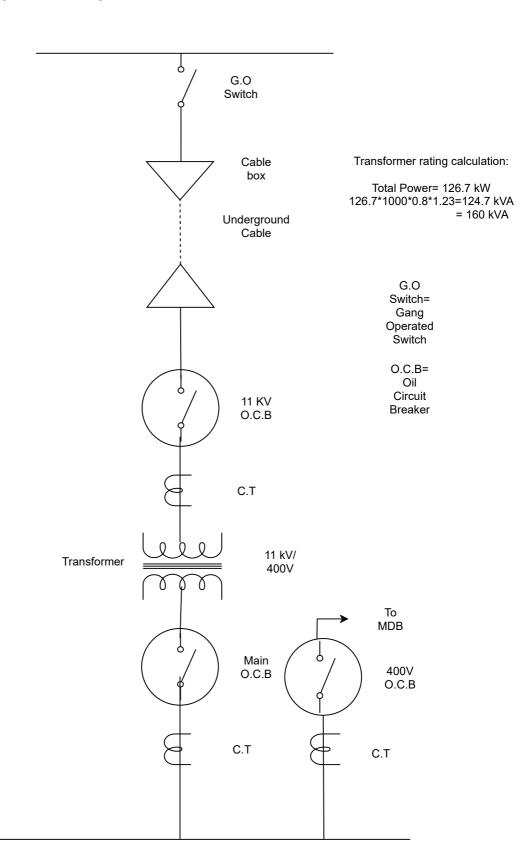Single Line Diagram of 11kV / 400V Indoor Substation



Lightning Protection of the Building

Air Spike

Lightning rod



Roof Conductor

To convert air spikes.



Down Conductor

A copper strip that connects roof

conductor to earthing rod



Earth electrode

Buried under the ground that lets lightning energy flow to the earth

Earthing System of the Building

Earth Continuity Conductor (ECC)

Transfers leakage current from faulty equipment to Earth




Earth Lead (EL)

To convert ECC Earth electrode



Earth Electrode

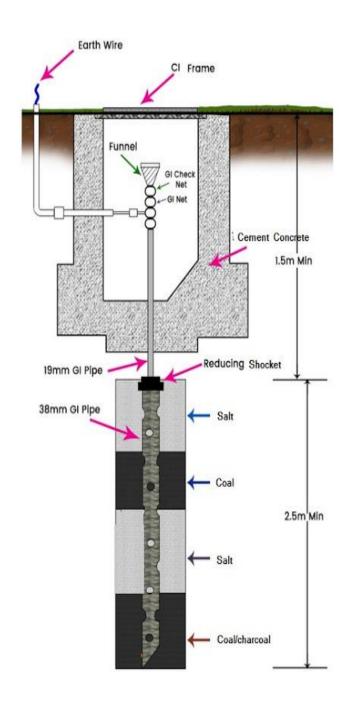Buried under the ground, lets the faulty current to Earth.



Earth resistance measured with 3 point method and is found to be less than 3Ω .

Light Calculation of Dining Room

Room Specifications


Room dimension = 20'*15'

Required illumination= 70 Lux

Wattage of light = 10 W

Room height= 3.25 m

Working distance = 0.5 m

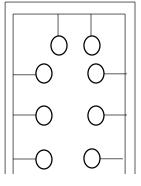

Living Room 20'*15'

Using 70-50-20, UF=0.42 and LLF=0.8

No. of lambs= (70*6.09*4.57) / (806*0.42*0.8)

Distance between lights= 20'/(3+1)

= 4'

PV System Calculation

Appliance	Total Number	Wattage	Hour of Operation	Energy (Wh)
CFL Lamp	14	26	8	2912
Fluorescent Lamp	7	40	6	1680
Fan	5	80	12	4800
Ceiling Light	3	60	10	1800
Mirror Light	3	40	2	720
Television	2	200	6	2400

= 14312 Wh

For 10 stored building with 5% laod,

= 7156 Wh

Total Power per floor= (14*26) + (7*40) + (5*80) + (3*60) + (3*40) + (2*200)

For 10 stored building with 5% laod,

= 862 Wh

BP Solar MSX- 300 Module

Max Power= 300 (STP)

Max Current= 8.35 Amp

Max voltage= 36 V

Nominal Output Voltage= 36V

 V_{oc} = 43.4 V and I_{ac} = 9.5A